

Practical Manual
Lab: Network Theory

Electronics & Communication Engg. (ECE)



RAO PAHALD SINGH GROUP OF INSTITUTIONS

BALANA(MOHINDER GARH)123029

Prepared By.

Mr.Manoj Saini

Checked By.

Mr.Pawan Kumar

EXPERIMENT NO :1

AIM:

To find resonance frequency , Bandwidth , Q - factor of RLC series circuit

APPARATUS REQUIRED :

Power Supply, Function Generator, CRO, Series Resonance kit,
Connecting Leads.

PRECAUTIONS :

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Handle the CRO carefully.
- d) Note the readings carefully.

BRIEF THEORY :

The ckt. is said to be in resonance if the current is in phase with the applied Voltage . Thus at Resonance, the equivalent complex impedance of the ckt. consists of only resistance R. Since V & I are in phase, the power factor of resonant ckt. is unity.

The total impedance for the series RLC ckt. is

CIRCUIT DIAGRAM:

POCEDURE :

- a) Make connection as per the circuit diagram & switch 'ON' the supply.
- b) Feed the sine wave to the I/P terminal from function generator.

- c) Adjust the peak to peak voltage of sine wave to 10V (V1) & frequency to 1 KHz.
- d) O/P is connected to CRO.
- e) Now change the I/P freq. with the help of function generator & note down the corresponding
- f) Reading of O/P voltage from CRO screen.
- g) At resonance freq. O/P will be max.
- h) Plot the graph between freq. & O/P voltage. Calculate resonance freq., band width & Q.

OBSERVATION TABLE:

GRAPH:

RESULT/CONCLUSIONS:

The resonance frequency , bandwidth & Q - factor of RLC series circuit has been calculated

DISCUSSIONS:

At cut-off frequencies the voltage becomes $1/\sqrt{2}$

EXPERIMENT NO : 2

AIM:

To study and plot the transient response of RL circuit

APPARATUS REQUIRED :

Power Supply, Circuit Board Kit., CRO, Function Generator,

Connecting Leads

PRECAUTIONS :

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Handle the CRO carefully.
- d) Note the readings carefully.

BRIEF THEORY :

Let switch K be at position 1. When it is switched to 2 then the =n becomes

$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{i} = -R/L dt$$

Integrating & then taking log on both sides

$$\log i = -R t/L + \log c \quad \text{where } c \text{ is constant}$$

$$\text{or, } \log i = -Rt / L + \log c$$

$$\text{or, } i = c e$$

$$-Rt/l \quad \text{-----}(1)$$

This is the general solution of RL circuit if the value of C2 is calculated

then the result is known as particular solution.

Just before switching at $t = 0$,

$$i(0) = V / R$$

P

Putting in equation (1)

$$I(0) = C$$

e

, C

$$= V / R$$

$$V / R$$

2

2

Particular solution is

$$i = V / R e$$

CIRCUIT DIAGRAM:

PROCEDURE:-

- a) Connect the circuit according to the fig. & switch 'ON' the Supply.
- b) Feed square wave from function generator to the I/P terminal of the circuit
- c) Connect the CRO to the O/P terminal & note down the O/P wave.
- d) Draw the I/P & O/P wave on the graph paper.

GRAPH:

RESULT/CONCLUSIONS:

Transient response of RL circuit has been studied and the results obtained are shown on the graph.

EXPERIMENT NO – 3

AIM :-

To study and plot the transient response of RC circuit.

APPARATUS REQUIRED :

Power Supply, Circuit Board Kit., CRO, Function Generator,

Connecting Leads.

PRECAUTIONS :

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Handle the CRO carefully.
- d) Note the readings carefully.

BRIEF THEORY :

Let initially the K is at 1, if it is moved to position 2, then apply KVL,

$$\frac{1}{C} \int i dt + Ri = V$$

Differentiating w.r.t 't'

$$\frac{1}{C} i + R \frac{di}{dt} = 0$$

$$R \frac{di}{dt} = -\frac{1}{C} i$$

$$\frac{di}{i} = -\frac{1}{RC} dt$$

Integrating w.r.t to 'i' & then taking log on both sides

$$\log i = -\frac{1}{RC} t + C$$

$$2$$

$$i = C$$

$$e^{-}$$

----- (1)

t/CR

2

On putting $I = V/R$ in equation (1)

e

$V/R = C$

$-t/CR$

2

At $t = 0$, C

$= V/R$

2

$i = V/R e$

$-t/RC$

CIRCUIT DIAGRAM:

PROCEDURE :

- a) Connect the ckt. according to the fig. & switch 'ON' the supply .
- b) Feed square wave from function generator to the I/P terminal of the ckt.
- c) Connect the CRO to the O/P terminal & note down the O/P wave .
- d) Draw the I/P & O/P wave on the graph paper .

GRAPH:

RESULT/CONCLUSIONS:

Transient response of RC circuit has been studied and the results obtained are shown on the graph.

DISCUSSION:

The capacitor charges and discharges within one minute.

EXPERIMENT NO : 4

AIM:

To calculate and verify 'Z' parameters of two-port network

APPARATUS REQUIRED :

Power Supply, Bread Board, Five resistances, Connecting Leads

Voltmeter , Ammeter

PRECAUTIONS:

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Note the readings carefully.

BRIEF THEORY :

In Z parameters of a two-port , the input & output voltages V_1

& V_2

can be

$V_1 = Z_{11}I_1 + Z_{12}I_2$

$V_2 = Z_{21}I_1 + Z_{22}I_2$

expressed in terms of input & output currents I_1

& I_2

. Out of four variables (i.e V_1, V_2, I_1, I_2

, V_1

, I_1

, I_2

)

1

2

1

2

1

2

V

& V

are dependent variables whereas I

& I

are independent variables .Thus ,

1

2

1

2

V

= Z

I

+ Z

I

-----(1)

1

11

1

12

2

V

= Z

I

+ Z

I

----(2)

2

21

1

22

2

Here Z

& Z

are the input & output driving point impedances while Z

& Z

are the reverse

11

22

12

21

& forward transfer impedances.

CIRCUIT DIAGRAM:

PROCEDURE:

- a) Connect the circuit as shown in fig. & switch 'ON' the experimental board.
- b) First open the O/P terminal & supply 5V to I/P terminal. Measure O/P Voltage & I/P Current
- c) Secondly, open the I/P terminal & supply 5V to O/P terminal. Measure I/P Voltage & O/P Current using Multimeter.
- d) Calculate the values of Z parameter using Equation (1) & (2).
- e) Switch 'OFF' the supply after taking the readings.

OBSERVATION TABLE:

When I/P is open ckted When O/P is open ckted

S.N.O V

V

I

V

V

I

2

1

2

2

1

1

SAMPLE CALCULATION:

(1) When O/P is open circuited i.e. I

= 0

2

Z

= V

/I

Z

=V

/I

11

1

1

21

2

1

(2) When I/P is open circuited i.e. I

= 0

I

Z

= V

/I

Z

= V

/I

12

1

2

22

2

2

RESULT/CONCLUSION:

The Z-parameters of the two port network has been calculated and verified .

DISCUSSION:

The Z-parameters are open circuit parameters

EXPERIMENT NO : 5

AIM:

To calculate and verify 'Y' parameters of two-port network

APPARATUS REQUIRED :

.Power supply, Bread Board, Five resistances, Connecting Leads,
Voltmeter , Ammeter .

PRECAUTIONS :

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Note the readings carefully.

BRIEF THEORY :

In Y parameters of a two-port , the input & output currents I_1

& I_2

can be

I_1

I_2

expressed in terms of input & output voltages V_1

& V_2

. Out of four variables (i.e I_1

, I_2

, V_1

V_2

I_1

2

1

2

1,

2

) I

& I

are dependent variables whereas V

& V

are independent variables.

1

2

1

2

I

= Y

V

+ Y

V

----- (1)

1

11

1

12

2

$$I = Y \frac{V}{V + Y} \quad (2)$$

2

21

1

22

2

Here Y

& Y

are the input & output driving point admittances while Y

& Y

are the reverse

11

22

12

21

& forward transfer admittances.

CIRCUIT DIAGRAM:

PROCEDURE :

- a) Connect the circuit as shown in fig. & switch 'ON' the experimental board.
- b) First short the O/P terminal & supply 5V to I/P terminal. Measure O/P & I/P current
- c) Secondly, short the I/P terminal & supply 5V to O/P terminal. Measure I/P & O/P current using multimeter.
- d) Calculate the values of Y parameter using Eq. (1) & (2) .
- e) Switch 'off' the supply after taking the readings.

OBSERVATION TABLE:

When I/P is short cktd When O/P is short cktd

S.N.O V

1

1

V

1

1

2

1

2

1

1

2

SAMPLE CALCULATION:

(1) When O/P is short circuited i.e. V

= 0

2

Y

= I

/V

Y

= I

/V

11

1

1

21

2

1

(2) When I/P is short circuited i.e. V

= 0

I

Y

= I

/V

Y

= I

/V

12

1

2

22

2

2

RESULT/CONCLUSION:

The Y-parameters of the two port network has been calculated and verified .

DISCUSSION:

The Y-parameters are short circuit parameters

EXPERIMENT NO: 6

AIM:

To calculate and verify 'ABCD' parameters of two-port network

APPARATUS REQUIRED:

Power Supply, Bread Board, Five resistances, Connecting Leads

Voltmeter, Ammeter.

PRECAUTIONS:

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Note the readings carefully.

BRIEF THEORY:

ABCD parameters are widely used in analysis of power transmission engineering where they are termed as “ Generalized Circuit Parameters” . ABCD parameters are also known as “Transmission Parameters”. In these parameters, the voltage & current at the sending end terminals can be expressed in terms of voltage & current at the receiving end.

Thus,

V_1

$= AV_2$

$+ B (-I_2)$

)

1

2

2

1

= CV

+ D (-I

)

1

2

2

Here “A” is called reverse voltage ratio, “B” is called transfer impedance “C” is called transfer admittance & “D” is called reverse current ratio.

CIRCUIT DIAGRAM:

PROCEDURE :

- a) Connect the circuit as shown in fig. & switch ‘ON’ the experimental board.
- b) First open the O/P terminal & supply 5V to I/P terminal. Measure O/P voltage & I/P current
- c) Secondly, short the O/P terminal & supply 5V to I/P terminal. Measure I/P & O/P current using multimeter.
- d) Calculate the A, B, C, & D parameters using the Eq. (1) & (2).

OBSERVATION TABLE:

When O/P is open ckted When O/P is short ckted

S.N.O V

V

I

V1 I

I

1

2

1

2

1

SAMPLE CALCULATION:

(1)When O/P is open circuited i.e. I2

= 0

A = V

/V

C = I

/V

1

2

1

2

(2) When O/P is short circuited i.e. V2

= 0

B = -V

/I

D = -I

/I

1

2

1

2

RESULT/CONCLUSION:

The ABCD-parameters of the two-port network has been calculated and verified.

DISCUSSION:

ABCD parameters are transmission parameters

EXPERIMENT NO : 7

AIM:

To determine equivalent parameters of parallel connection of two-port network

APPARATUS REQUIRED:

Power Supply, Bread Board, Five Resistances, Connecting Leads, Voltmeter, Ammeter

PRECAUTIONS:

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Note the readings carefully.

BRIEF THEORY:

Consider two port N/Ws connected in parallel so that they have common reference node, then the equation of the N/Ws A&B in terms of Y parameters are given by

Y

= Y

A + Y

B

11

11

11

Y

= Y

A + Y

B

12

12

12

Y

= Y

A + Y

B

21

21

21

Y

= Y

A + Y

B

22

22

22

Thus we see that each Y parameter of the parallel N/W is given as the sum of the corresponding parameters of the individual N/Ws.

CIRCUIT DIAGRAM:

PROCEDURE:

- a) Connect the N/Ws A&B separately on the Bread board according to the fig.
- b) Take the Reading according to the observation table & calculate Y parameters
- c) for both N/Ws & add them.
- d) Connect the two N/Ws A&B in parallel & take the readings.
- e) Calculate the Y parameters of l1el connected N/Ws.
- f) Verify that the sum of parameters of A&B N/Ws is equal to the parameters of
- g) parallel connected N/Ws.

OBSERVATION TABLE:

When I/P is short cktd When O/P is short cktd

S.N.O V

1

1

V

1

1

2

1

2

1

1

2

SAMPLE CALCULATION:

(3) When O/P is short circuited i.e. V

= 0

2

Y

= I

/V

Y

= I

/V

11

1

1

21

2

1

(4) When I/P is short circuited i.e. V

= 0

1

Y

= I

/V

Y₂₂ = I

/V

12

1

2

2

RESULT/CONCLUSION:

The Y-parameters of parallel connection of two-port network has been determined .

DISCUSSION:

The overall Y-parameters of a parallel connection is equal to sum of individual network parameters.

EXPERIMENT NO : 8

AIM:

To plot the frequency response of High pass filter and determine the half-power frequency

APPARATUS REQUIRED:

Power Supply, Filter ckt. Kit, Resistances, Audio Frequency Generator, two voltmeters .

BRIEF THEORY :

A HP filter attenuates all frequencies below a designated cut-off frequency

f_c

, & passes all freq. above f_c

. Thus the pass band of this filter is the freq. range above f_c & the

stop

band

is the freq. range below f_c . An attenuation characteristic of a HP filter is shown in fig.

f_c f

CIRCUIT DIAGRAM:

PROCEDURE:

- a) Connect the circuit. according to the circuit diagram
- b) Connect the audio signal generator with 600 Ω source impedance to the I/P of the filter terminate that the O/P with a 6000 Ω resistive load.
- c) Connect two voltmeter at I/P & O/P terminal.
- d) Set the I/P voltage to app. 1Vrms at 1 KHz.
- e) Vary the I/P freq. from 0 to 10KHz in small steps. Measure I/P& O/P voltage at each Step.
- f) Take more reading where the attenuation roll off is predominant.
- h) Draw the graph.

OBSERVATION TABLE:

S.N.O Frequency (KHz) I/P Voltage

O/P Voltage

$a = 20 \log V$

/V

2

1

V

(Volts)

V

(Volts)

1

2

SAMPLE CALCULATION:

$a = 20 \log V$

/V

2

1

RESULT/CONCLUSION:

The frequency response of High Pass Filter has been plotted on the graph .Also its half-power frequencies has been determined.

DISCUSSION:

High Pass Filter passes the frequencies above cut-off frequencies.

d) Take output carefully.

EXPERIMENT NO: 9

AIM:

To plot the frequency response of Low pass filter and determine the half-power frequency

APPARATUS REQUIRED:

Power Supply, Filter circuit Kit, Resistances, Audio

Frequency Generator, two Voltmeters.

PRECAUTIONS:

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Handle the CRO carefully.
- d) Note the readings carefully.
- e) Take output carefully.

BRIEF THEORY:

A Low pass filter is one which passes without attenuation all frequencies up to the cut-off frequency f_c

& simultaneously attenuates all other frequencies greater than f_c

.

c

c

The attenuation characteristic of an ideal L P filter is shown in fig.

This filter transmits all frequencies from zero to cut-off frequency. The band is called pass band.

The frequency range over which transmission does not take place is called the stop band.

f

$$= \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

CIRCUIT DIAGRAM:

PROCEDURE:

- a) Connect the ckt. according to the ckt. diagram
- b) Connect the audio signal generator with 600Ω source impedance to the I/P of the filter.
Terminate the O/P with a 600Ω resistive load.
- c) Connect two voltmeters at I/P & O/P terminal.
- d) Set the I/P voltage to app. 1V
at 1 KHz.
rms
- e) Vary the I/P freq. from 0 to 10KHz in small steps. Measure I/P & O/P voltage at each

step.

f) Take more reading where the attenuation roll off is predominant.

g) Draw the graph.

OBSERVATION TABLE:

S.N.O Frequency (KHz) I/P Voltage

O/P Voltage

$a = 20 \log V$

/V

2

1

V

(Volts)

V

(Volts)

1

2

SAMPLE CALCULATION:

$a = 20 \log V$

/V

2

1

GRAPH:

RESULT/CONCLUSION:

The frequency response of Low Pass Filter has been plotted on the graph. Also its half-power frequencies has been determined.

DISCUSSION:

Low Pass Filter passes the frequencies below cut-off frequencies

EXPERIMENT NO : 10

AIM:

To study frequency response of Band pass filter.

APPARATUS REQUIRED:

Power Supply, Filter ckt. Kit, Resistances, Audio

Frequency Generator, two Voltmeters.

PRECAUTIONS:

- a) Make the connections according to the circuit diagram. Power supply should be switched off.
- b) Connections should be tight.
- c) Handle the CRO carefully.
- d) Note the readings carefully.
- e) Take output carefully.

BRIEF THEORY:

A band pass filter passes freq. Between two designated cut-Off fr eq.& attenuates all other freq. . BPF has two cut-off freq. As shown in fig. f is called lower cut-off

1

freq.& f

is upper cut-off freq.

2

CIRCUIT DIAGRAM:

PROCEDURE:

- a) Connect the ckt. according to the ckt. Diagram
- b) Connect the audio signal generator with 600Ω source impedance to the I/P of the filter terminate that the O/P with a 600Ω resistive load.
- c) Connect two voltmeter at I/P & O/P terminal.
- d) Set the I/P voltage to app. 1V_{rms} at 1KHz.
- e) Vary the I/P freq. from 0 to 10KHz in small steps. Measure I/P & O/P voltage at each step.
- f) Take more reading where the attenuation roll off is predominant.
- g) Draw the graph.

OBSERVATION TABLE:

S.N.O Frequency (KHz) I/P Voltage

O/P Voltage

$a = 20 \log V$

/V

2

1

V

(Volts)

V

(Volts)

1

2

SAMPLE CALCULATION:

$$a = 20 \log V$$

/V

2

1

GRAPH:

RESULT/CONCLUSION:

The frequency response of Band Pass Filter has been plotted on the graph and its bandwidth has been calculated .

DISCUSSION:

The Band Pass Filter is obtained by connecting Low Pass and High Pass Filter in cascade provided that the Low Pass Filter has cut-off frequency higher than High Pass Filter.